





Failed cell detection circuit

Frank Davies

September 2, 2014

-
- Orbiter

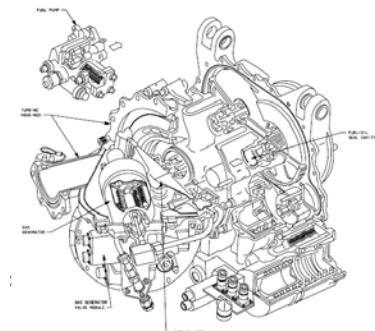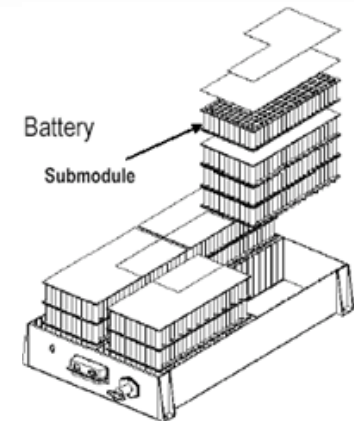



In batteries built with many parallel strings of cells it is complicated to detect non-functional or damaged strings.

- One bad string in a large number of parallel strings makes a small percentage difference but significantly affects safety margins.
 - Faulty strings can be detected by monitoring individual currents during load tests, but monitoring many parallel strings gets complicated.
 - If each string has a resistive current shunt, many wires must run from the battery to the equipment used to test it. In a high voltage, high power battery, these wires present safety concerns because they are not isolated from the high voltage buss.
 - Having isolated current sensors solves the safety concerns, but such sensors are bulky and do not solve the problem of a large number of sensor wires exiting the battery.
- Technology covered by NASA patent 8,570,047



Advantages:


- Easy detection of single string fault among many strings.
- Minimal components added to battery (one toroid core per string plus winding wires)
- Core saturation minimizes effects on battery impedance when battery is supplying nominal load current.
- Electrical isolation intrinsic to design.
- No effect on battery DC and low frequency impedance.

Disadvantages:

- Small effect on battery impedance at high frequencies.
- Extra connector on battery is necessary.


Pre-operational check

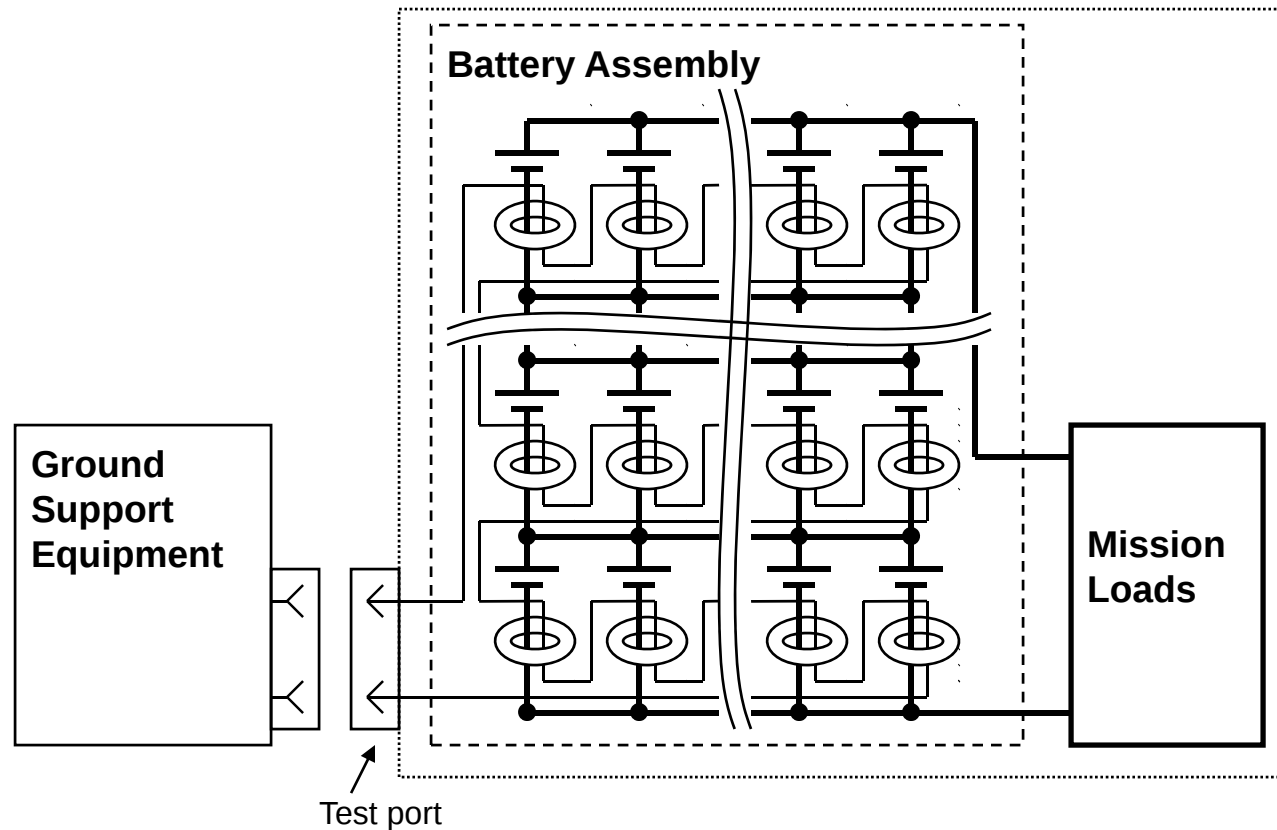For operations and missions where battery mass and size are critical and opportunities for maintenance or reconfiguration during the mission are limited.



Continuous monitoring:



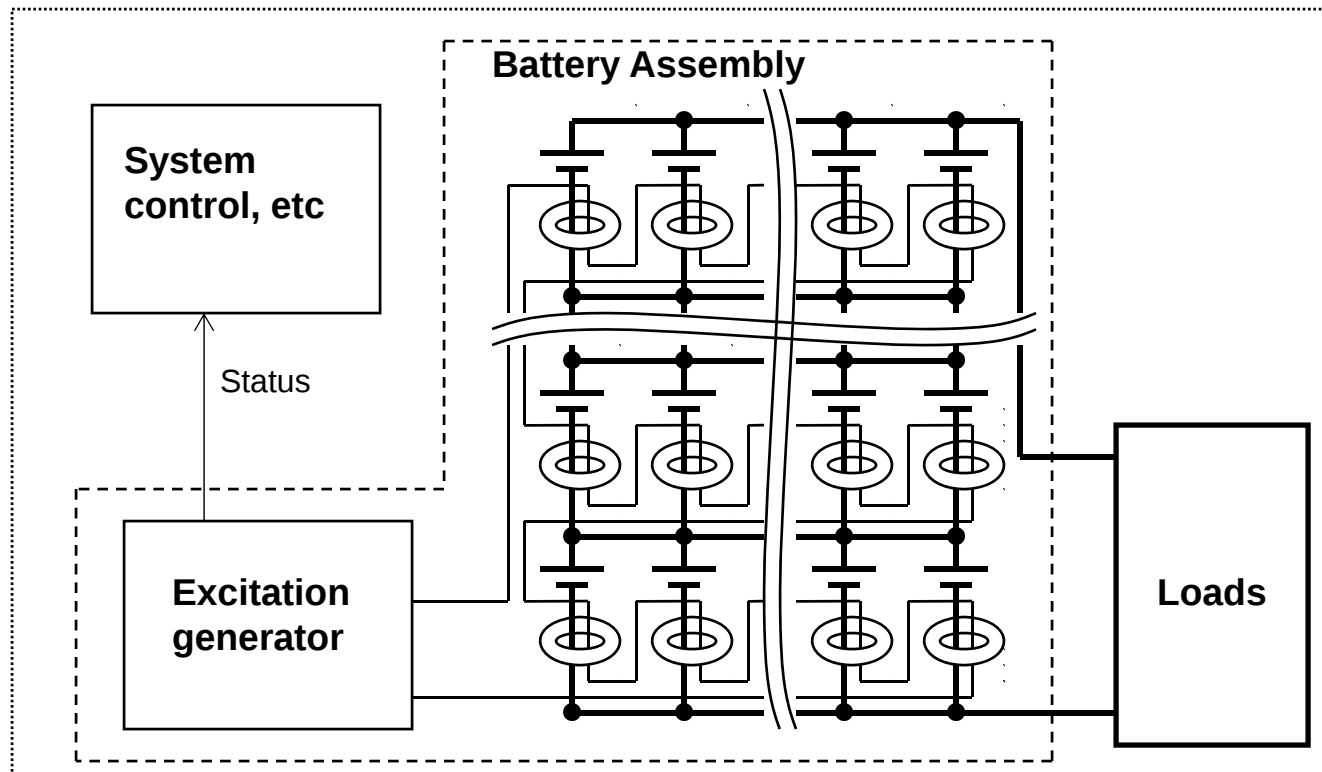
For operations without a distinct pre-operational test phase, where continuous monitoring is merited because maintenance or reconfiguration can be performed in response to a detected problem.




10 cell prototype



Schematic of 10 cell test battery:

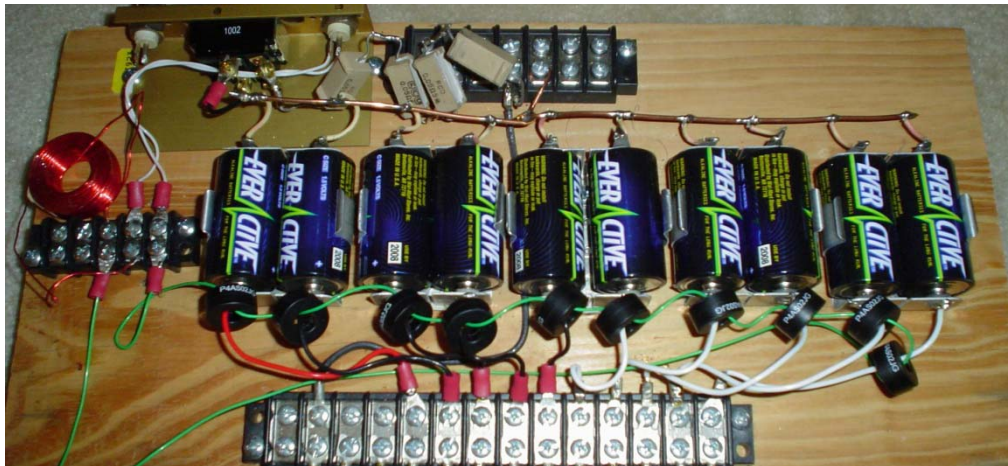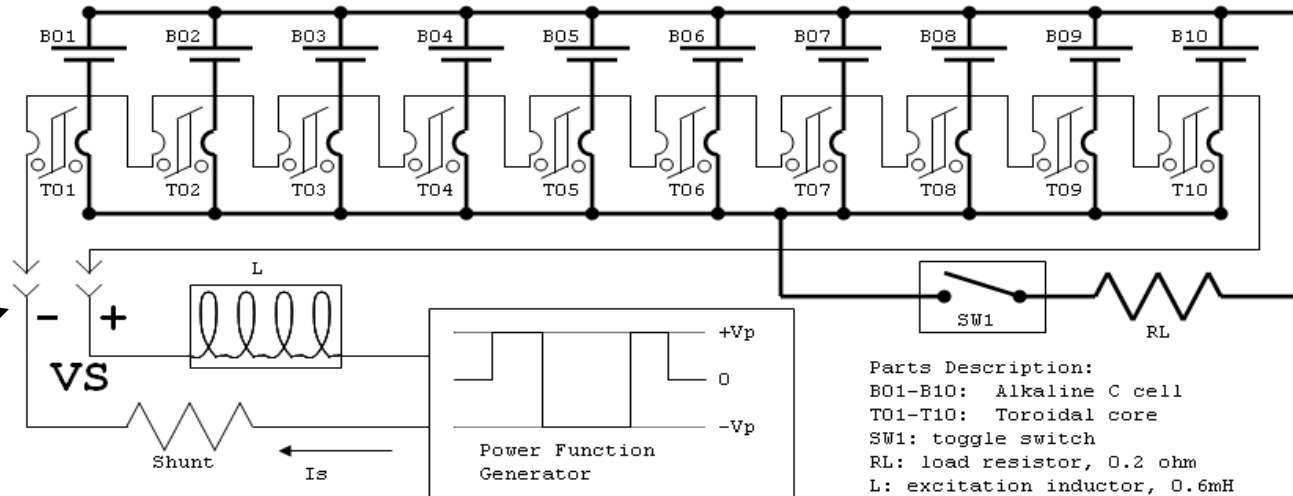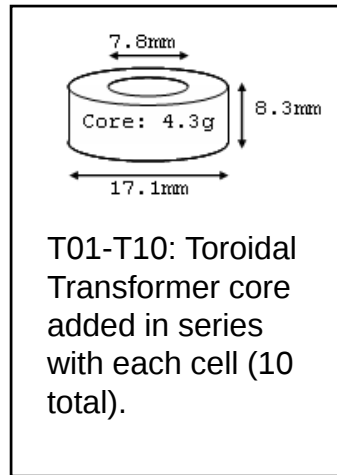

VS pulse with all cells good:


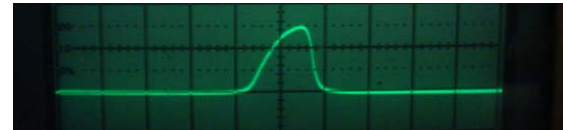


VS pulse w/ one cell failed open:



Pulse from failed cell.

75 cell prototype (180Ahrs)

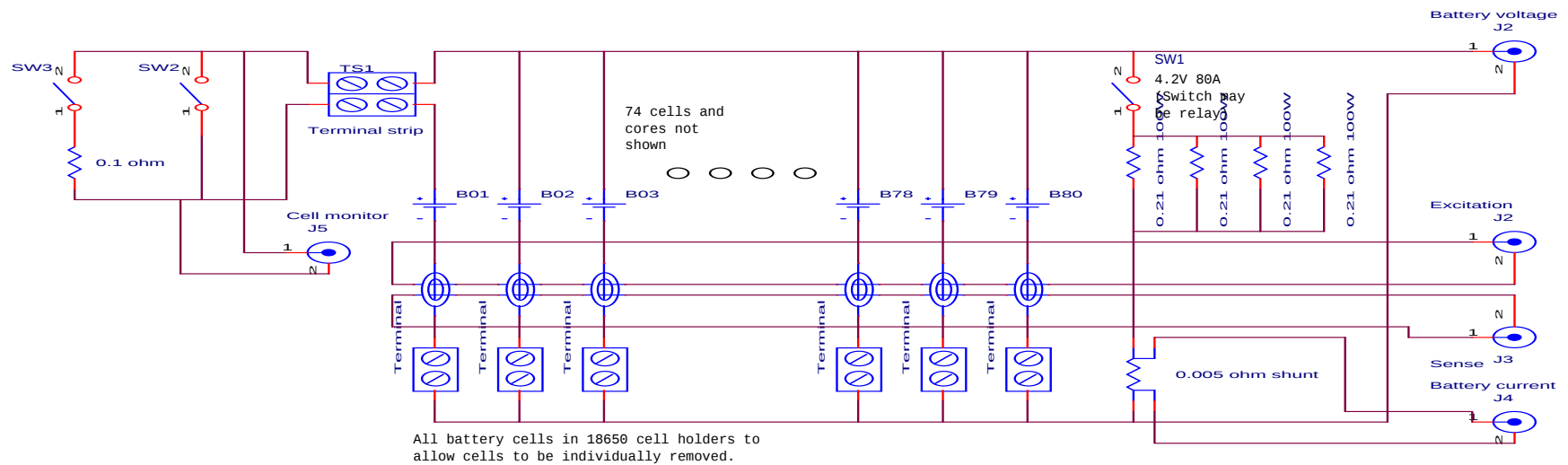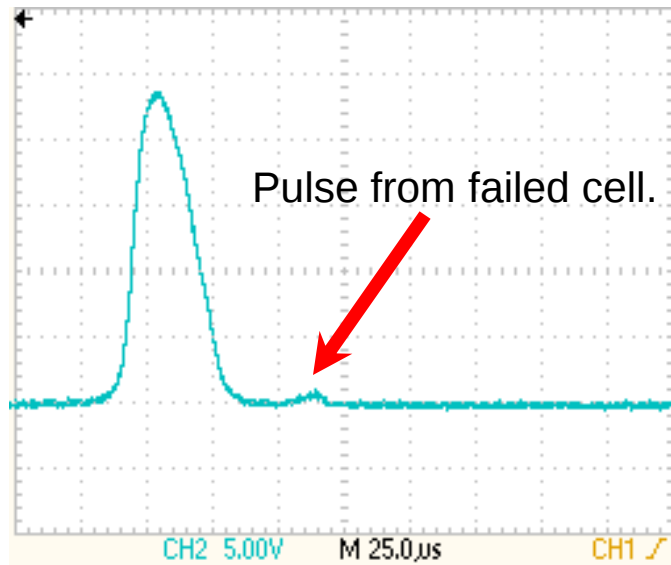


Operating principle: Single string operation



Basic principle: A toroidal core can act as a sensor that turns a current level into the timing of a pulse.


SW1 open:

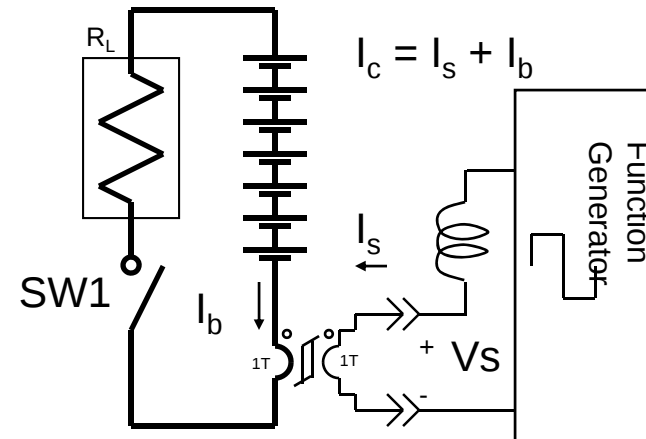1. No current through battery and resistor ($I_b = 0$).
2. Function generator and inductor make triangular current waveform.
3. Pulses on V_s right after zero crossings of sense current (I_s).



SW1 closed:

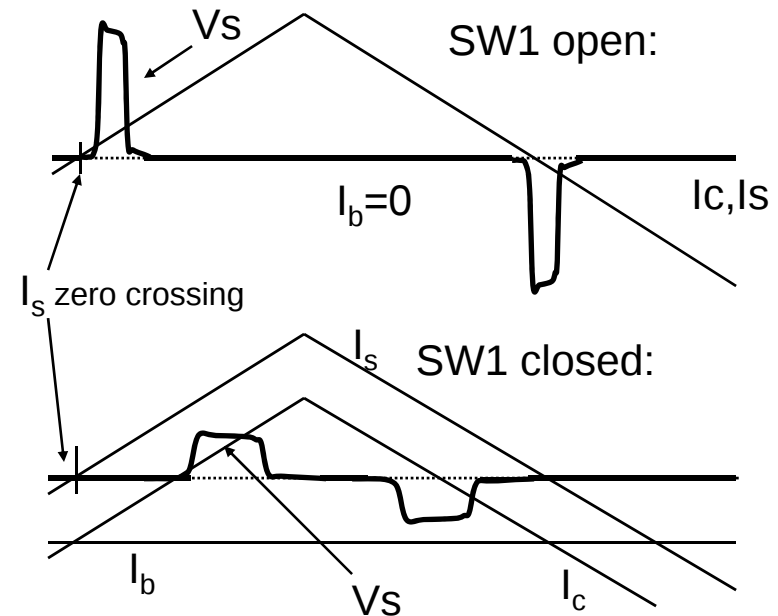
1. DC current through battery and load.
2. DC current adds to I_s to shift zero crossings of magnetizing current (I_c).
3. Pulse shape changed by interaction with battery and load impedance.
4. Timing of pulse (delay from I_s zero crossing) changed due to DC battery current.



Operating principle: multiple strings



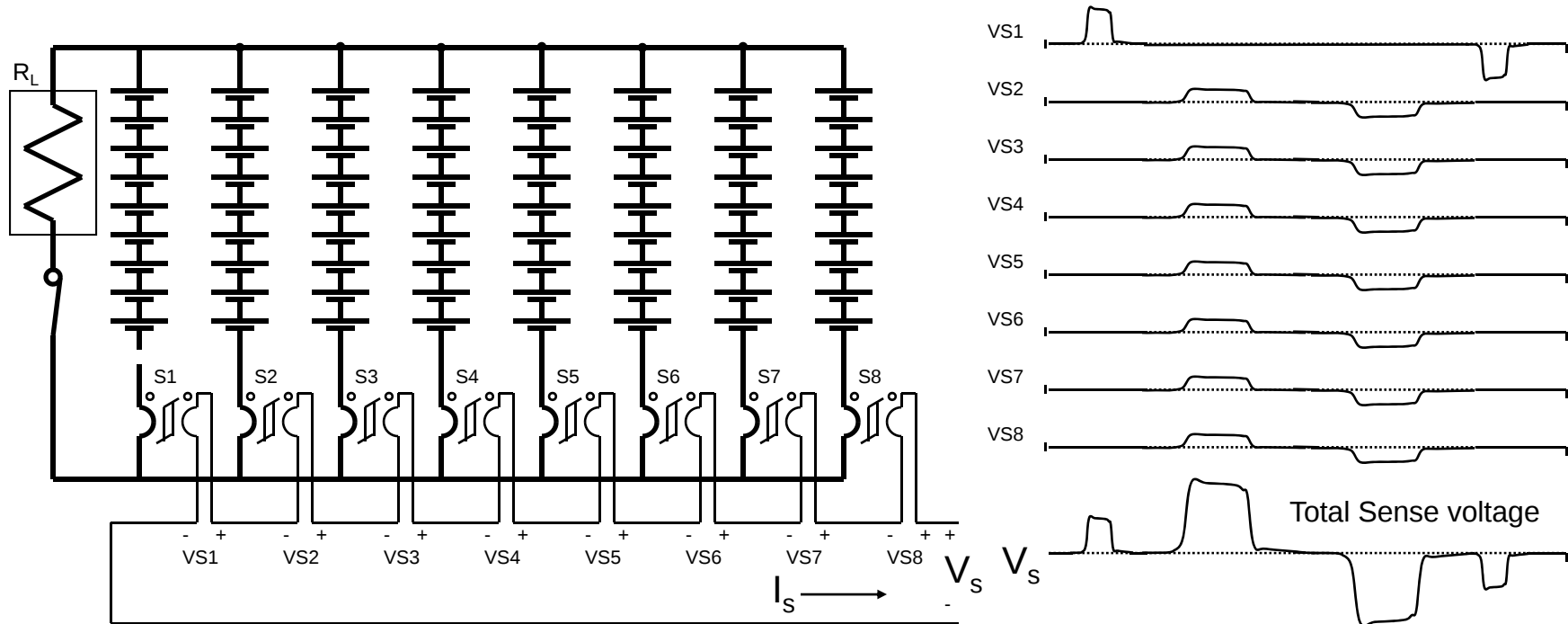Basic principle: A cell string with a problem produces a pulse at a different time than all the good pulses.



Note:

1. Fault present (open circuit) in string 1.
2. Load current splits up between strings

