



## Wideband Reconfigurable Harmonically Tuned GaN SSPA for Cognitive Radios

Seth W. Waldstein
The University of Cincinnati-Main Campus

Miguel A. Barbosa Kortright University of Puerto Rico, Mayagüez Campus

Rainee N. Simons
NASA Glenn Research Center

### Outline

**Introduction - Motivation** 

**Benefits & Challenges** 

Wide-Band Reconfigurable Harmonically Tuned Power Amplifier

- Inverse Class-F Design
- Amplifier Fabrication and Results
- Thermal Management
- Dual-Band Multi-Network Design

### **Power Variability**

- Hybrid Coupler
- Balanced Amplifier

**Conclusions and Acknowledgements** 

## Introduction - Motivation

- Spectrum management issues due to growing user community
  - Congestion in the X-Band space-to-ground data links is creating the need for cognitive radio capabilities

What do we need from transmit power amplifiers in a cognitive communication system?

- I. Re-configurability
  - High output power; without sacrificing efficiency
  - Operating frequency; without sacrificing efficiency
- **II.** Linearity

## Benefits

### **Higher Efficiency Means**

- Saved DC power
- Decreased Heat
  - Efficiency is lost primarily through power dissipation within the transistor junction and conductor losses.
  - Improved Thermal Reliability

### Potential to Enable Low Cost Cognitive Telemetry:

Avoids the need for multiple T<sub>x</sub> and R<sub>x</sub> modules

### **Applications include:**

- NASA Missions
- Small Satellites and Spacecraft
- Military Unmanned Air Vehicles
- Commercial/Amateur Cubesats

**Decrease in Heat Sink Mass** 

## Challenges

### **Efficiency**

• High Efficiency SSPA's require harmonic tuning - such as Class-F and Inverse Class-F designs. Matching circuit is complex and inherently narrow band.

### **Wideband Devices**

 Class-F type wideband harmonic tuning techniques used at lower frequencies are unrealizable at X-band


### **Power Variability**

Amplifiers efficiency drops off when operating below saturation

### **GaN Transistor Frequency Limitation**


- Achieving max PAE with Class-F type amplifiers requires  $F_T > 3^{rd}$  harmonic
- Current commercially available transistors have an F<sub>T</sub> of 18 GHz
- High F<sub>T</sub> of GaN HEMTs comes at the expense of feature size and power density
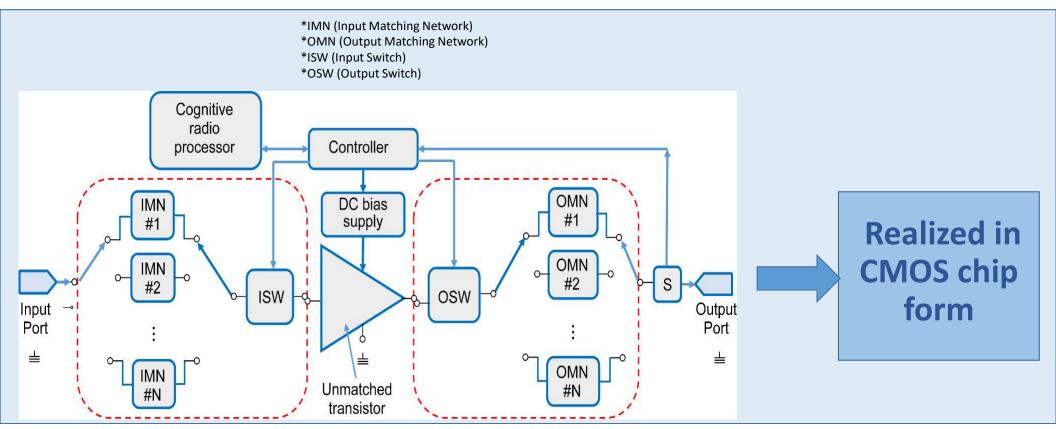
## Wide-Band Reconfigurable Harmonically Tuned PA




Design to provide wideband high efficiency using multinetwork tuning

## Inverse Class-F GaN SSPA at X-Band

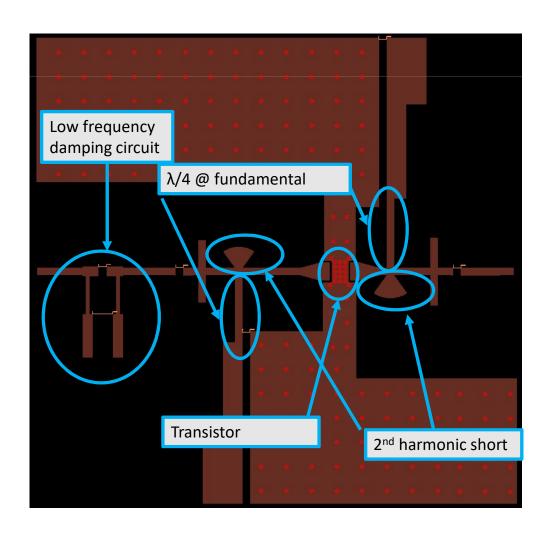
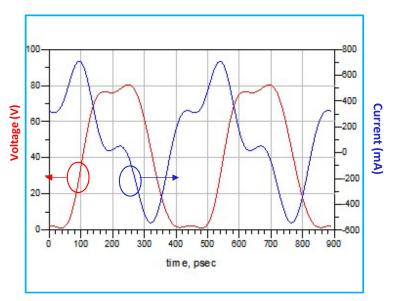
# Harmonics are reflected to reshape the voltage and current waveform at the drain




## Fabricated Inverse Class-F Amplifier

Low Freq DC Drain Stability Bias Circuit GaN **Transistor** 0 Parallel RL RF Output Gate Bias Choke DC Gate Input

Transistor: Cree CGHV1F006S 6W, DC-18 GHz, 40V, GaN HEMT

Substrate height, h = 0.02 inch &  $\varepsilon_r$  = 3.0


### Tuning of Inverse Class-F Amplifier

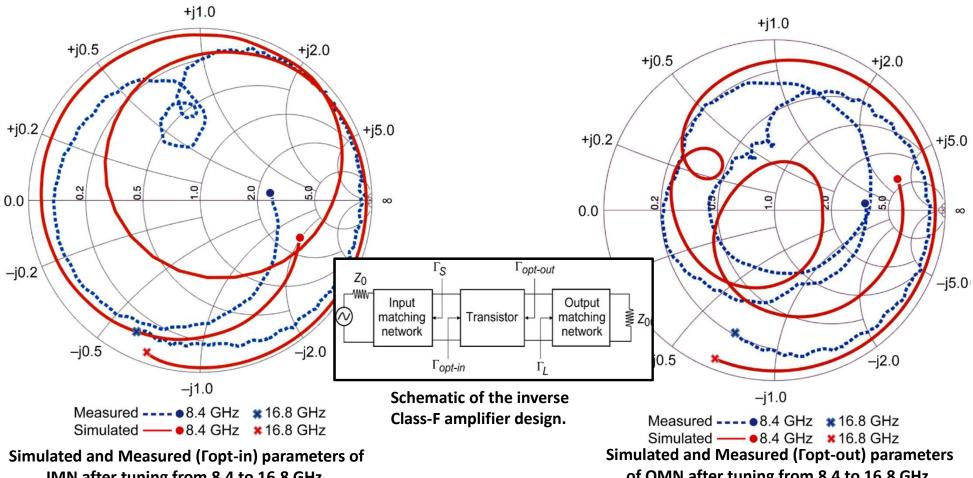


IMN after tuning from 8.4 to 16.8 GHz.

of OMN after tuning from 8.4 to 16.8 GHz.
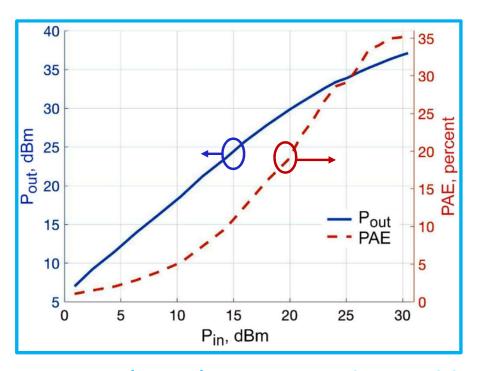
## Inverse Class-F P<sub>out</sub>, PAE, Gain and VSWR



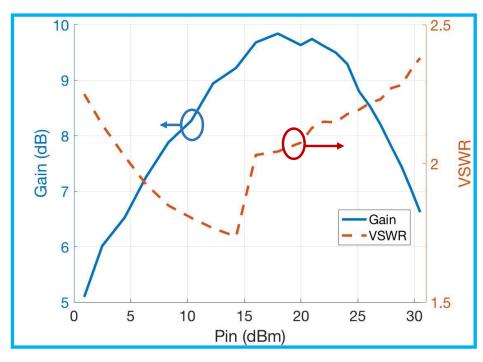
Measured  $P_{out}$  and PAE vs.  $P_{in}$   $V_{DS}$  = 40 V,  $V_{GS}$  = -3.2 V and frequency = 8.45 GHz.




Measured gain and VSWR vs.  $P_{in}$ ;  $V_{DS}$  = 40 V,  $V_{GS}$  = -3.2 V, and frequency = 8.45 GHz

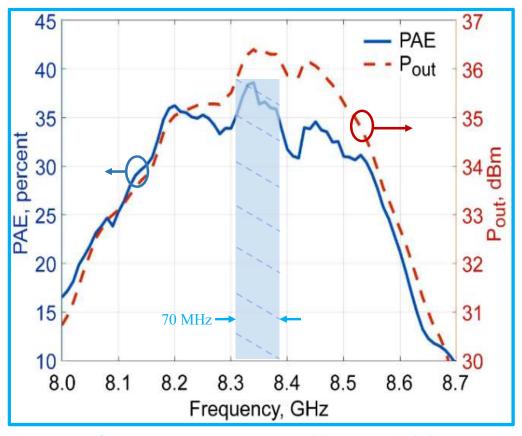
## Inverse Class-F Bandwidth

70 MHz bandwidth where Pout > 36 dBm and PAE > 35% 8.315 - 8.385 GHz



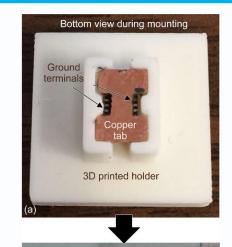
PAE and  $P_{out}$  vs. Frequency  $V_{DS} = 40$  V,  $V_{GS} = -3.2$  V;  $P_{in}$  ranges 21.5-30.35 dBm, VSWR ranges 2.4 -33




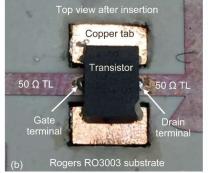

CW operation required direct contact between transistor belly and heat sink

## Thermal Management

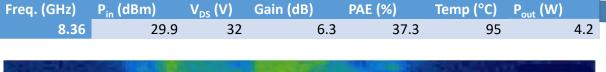

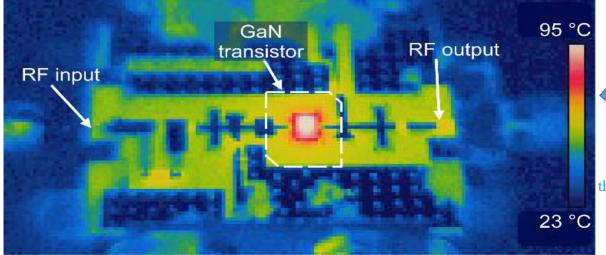

Operating conditions observed through thermal imaging


### Operating conditions of measured package temp = $95^{\circ}$ C:

DC Power Dissipation ≈ 7 W


 Data sheet indicates for package temperature of 95°C, the max allowed power dissipation is ≈ 9 W.

Hence, achieved thermal safety margin of ≈ 22%.

## Dual Band Multi-Network Design

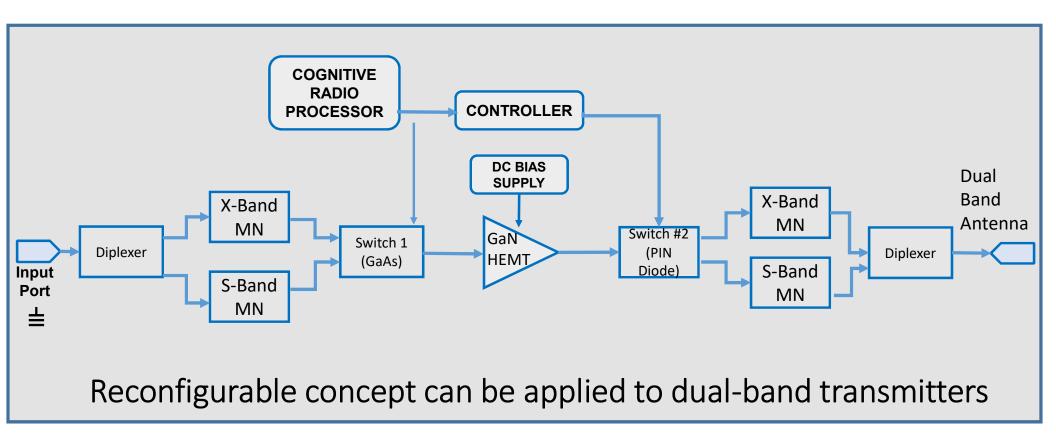

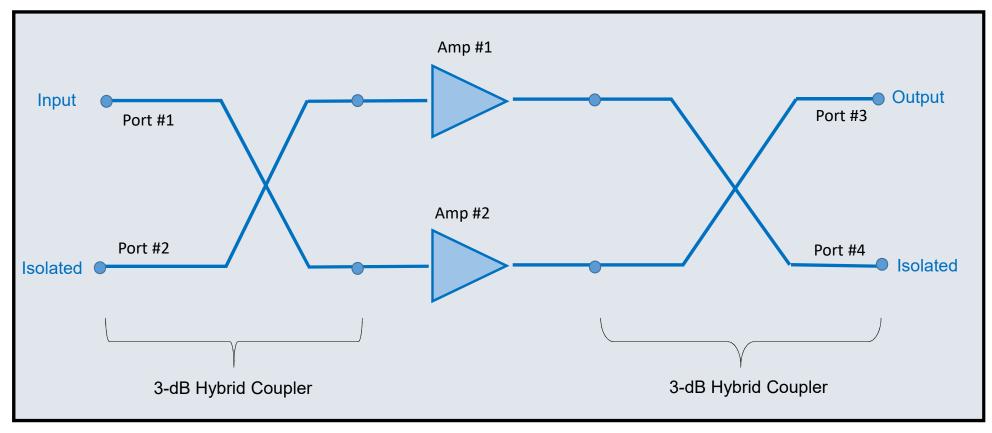
## Power Variability - Balanced Amplifier




Balanced Amplifier Circuit Topology
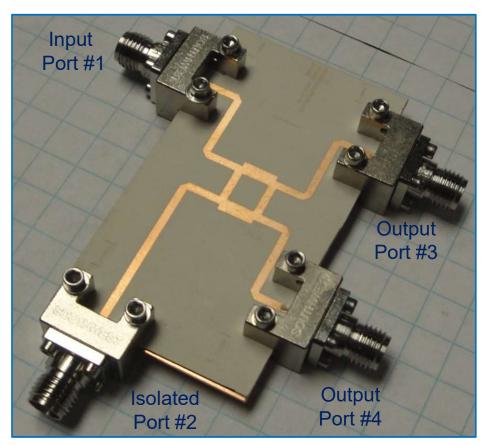
### Microstrip Branch Line 3-dB **Hybrid Coupler**




Substrate height, h = 0.02 inch &  $\varepsilon_r$  = 3.0

#### Measured vs Simulated Results

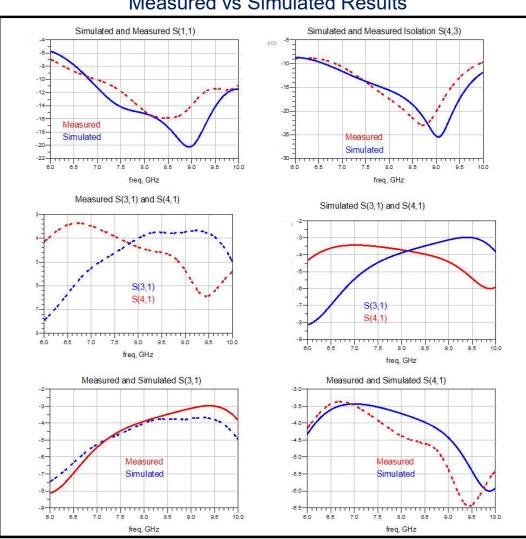


## Fabricated Balanced Amplifier

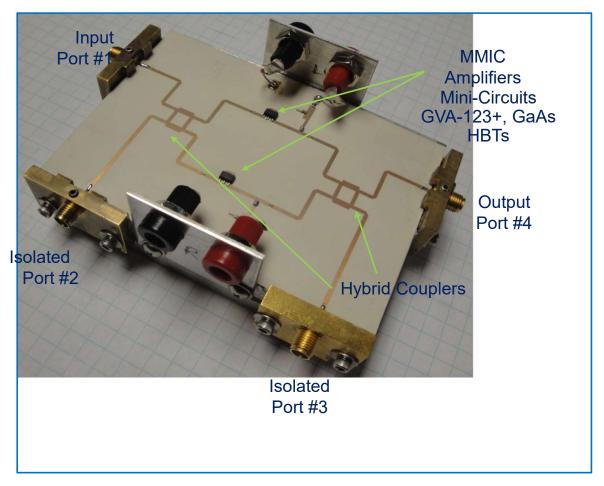
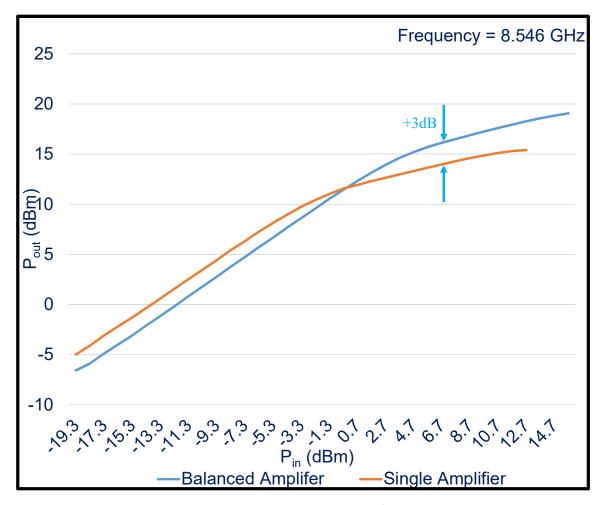
### P<sub>in</sub> vs. P<sub>out</sub> for Single & Balanced MMIC Amplifiers

Balanced amplifier provides a 3dB increase in output power over a single MMIC



Measured  $P_{out}$  vs.  $P_{in}$  with  $V_D = 5$  V and frequency = 8.546 GHz.

### Conclusion

- Challenges have been presented for achieving the desired high efficiency wide-band operation needed for a cognitive system at X-band
- An inverse Class-F GaN SSPA operating at 8.4 GHz has been shown to achieve 5W of output power at 40% PAE with a 70 MHz bandwidth of Pout > 36 dBm and PAE >35%.
- A reconfigurable harmonically tuned SSPA has been proposed and justified to provide wideband high efficiency
- A balanced amplifier has been presented for additional consideration in reconfigurable power topologies.