



Electronic Load Evaluation for Aerospace Power System Verification

Energy & Mobility
Technology, Systems, and Value Chain
Conference and Expo
September 12-15, 2023, Cleveland OH

NASA GRC: David Sadey, Nicolas Carbone, Kristen Boomer
HX5: Mike Kussmaul

- **History of Use**
- **Electronic Load Background**
- **Load Step Transient Verification**
- **Impedance & Stability Measurement**
- **Conclusion and Future Work**

History of Use (GRC PMAD Branch)



- **Electronic load (e-load) use limited for verification purposes at GRC**
 - Actual loads used to load down the system
 - Step-load transient testing performed with resistive load banks
 - Only allowed for steady-state tests & measurements
- **Use of these loads has produced misleading results**
 - Transient & Impedance results non-repeatable, non-representative
 - Core issues never truly understood
- **Current need to understand the issue**
 - Contractors are proposing use of electronic load banks for verification across projects
 - Use of resistive load banks becomes difficult as time progresses and systems grow to higher power and/or voltages

Electronic Load Background




- **Come in many different flavors**
 - Switched resistive, MOSFET controlled, hybrid, switched (converter)
 - Unidirectional and bidirectional
- **Advantages and disadvantages to each**
- **Goal of this presentation is not to fully evaluate each load type**
- **Goal is to identify possible limitations of electronic loads to be aware of for verification testing**
 - Important since electronic loads are being proposed for use in verification


Electronic Load Background (cont.)



 
- **Standard spacecraft loads are typically Constant Power (converters) or Resistive (heaters)**
- **E-load standard modes**



Constant Resistance

 

Constant Current

 

Constant Power



Constant Impedance

- **Spacecraft load types can only be represented by e-loads within a limited**
 - Bandwidth
 - Resolution




Load-Step Transient Verification

Evaluate Common Electronic Loads (Load Steps)



- **Initial thoughts prior to investigation**

 - Standard e-loads not suitable for load-step transients
- Most e-loads contain input capacitance
 - Capacitor discharges into load-steps
 - Discharge corrupts/mitigates load-step transient response



- **When are e-loads acceptable for load-step transient testing?**


- Strategy is to develop rule of thumb based on EPS performance vs. e-load bandwidth

Definitions and Approach




- **Source Bandwidth**

 - In this presentation, refers to frequency at which the peak source impedance occurs (ignoring leakage inductances)
- Characterized by source impedance measurement
- This is not the loop crossover frequency of the converter control loop



- **Load Bandwidth**

 
- Refers to the current/power/impedance response 3dB bandwidth
- Easily characterized based on transient response tests



Electronic Load Bandwidth < Source Bandwidth




 - **AMPS¹ DDCU² as source**
 - COTS³ e-load and resistive bank (FET switched) step loads
 - 1-2 / 2-1, 1-3 / 3-1 kW load steps, transient tests performed at 120Vdc



1. AMPS: Advanced Modular Power Systems
2. DDCU: DC-DC Converter Unit
3. COTS: Commercial-of-the-shelf


Load Step Transient Windows

 

Electronic Load Bandwidth < Source Bandwidth



 - Normalized (~120Vdc) / filtered 1-3kW load steps
- COTS e-load is too slow in all modes




This material is a work of the U.S. Government and is not subject to copyright protection in the United States

LTSpice Simulation Example of Load Bandwidth Changes



 - Load step transient results with varying rise times
 - Slow rise times represent bandwidth impacts of electronic loads



Electronic Load Bandwidth >> Source Bandwidth




- **AMPS DDCU as Source**


- Fast e-Load, Avtron resistive bank (FET step)
- Fast e-Load is much faster than AMPS DDCU in all control modes (>x10)



 
Electronic Load Bandwidth >> Source Bandwidth



 Electronic Load Bandwidth >> Source Bandwidth



LTSpice Simulation Results (Match)

 

Test Load Suitability for EPS Load-Step Transient Testing



- **What loads are suitable?**
 - Resistive or actual representative load (if known)
 - Resistive worst-case for general purpose interface
 - High bandwidth electronic loads
 - >10x Source Bandwidth General Rule of Thumb
 - 5-9x needs further engineering evaluation
- **Which loads aren't suitable?**
 - Low bandwidth electronic load (relative to source)
 - Loads with input capacitance > spec






Impedance & Stability Verification

Initial Impedance Thoughts



 - An interface's source impedance is impacted by the impedance of all of the parallel loads attached to that interface.
- When using an electronic load in place of actual constant power load, it must perform like the load it is trying to represent.




Load Impedance Primer





- **Resistive, Constant Current, Constant Power Loads**

 - Same EPS Transient Response
- Different impedance characteristics



  
Ideal Load Impedance with 100uF capacitance and no inductance





Characterizing an E-Load – Constant Power vs Constant Current



 
- When using an e-load in place of a “representative constant power load” it must be characterized correctly and its impedance must match the actual load itself.
- Example scenario: The source converter is stable with CC mode load and unstable with CP mode load.



  - **A/D's on digital loads can change the appearance of the load**
 - Occurs at 'very small signal' level within Quantization window(s)
 - CP load looks like a CC Load




 
- **So what? We are talking mV...**
 - mV is all some e-loads may see
 - Source impedance can be generalized as upstream parallel combination of all upstream sources and loads
- **Incorrect impedance measurements can occur due to e-load quantization effects**



Characterizing an E-Load – Constant Power vs Constant Current




- When using an e-load in place of a “representative constant power load” it must be characterized correctly and its impedance must match the actual load itself.
 - A load must be perturbed with a large enough injection signal during impedance measurements
 - The “quantized state” of some CP e-loads may give the appearance of a constant current load at very small signal
 - Voltage does not respond to the change in current because the change is too small
- Example scenario: The source converter appears stable with CC mode load, but is unstable with CP mode load.

  

Source and Load may be Stable in Steady-State!



 - Furthermore, without proper load impedance characterization a false sense of stability may be achieved for this electronic load + source combination
 - With light-loading this system is stable
 - With high-loading this system is unstable



Test Load Suitability for Stability Assessments



- **What loads are suitable?**
 - Actual representative load (if known)
 - Using standard DC-DC converters
 - Representative Filters
 - CP e-Loads with analog control circuitry (requires eng. evaluation)
- **Which loads have questionable suitability?**
 - Digital CP electronic loads
 - Quantization effects will impact measurements, CP loads may look like CC loads
 - Have inherent risk. Steps have to be taken to mitigate risk (follow on work/discussion).
- **Which loads aren't suitable?**
 - CC electronic loads
 - Will inherently mask instability problems
 - Any load without representative filtering

- **Detailed analysis and consideration must be taken into account when using e-loads for power system validation and verification**
 - General rule of thumb: e-Loads 10x faster than source for transient verification
 - CC loads cannot be used interchangeably with CP loads
 - A/D's on digital e-loads can affect appearance of the load at very small-signal levels
- **Detailed publication planned covering:**
 - Source converter loop-gain considerations vs. e-load bandwidth constraints
 - Varying test results
 - Simulation results with varying sources



Thanks to the Gateway Project and Revolutionary Vertical Lift Technology (RVLT) Project for the funding and support for this work.