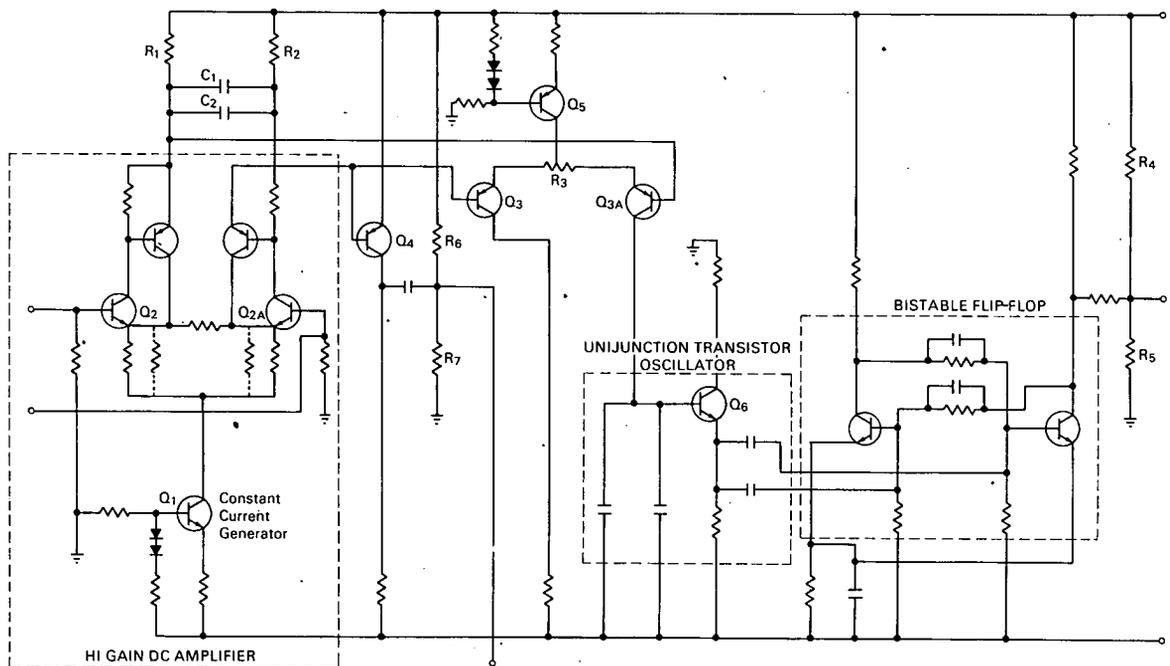


NASA TECH BRIEF



NASA Tech Briefs are issued to summarize specific innovations derived from the U.S. space program, to encourage their commercial application. Copies are available to the public at 15 cents each from the Clearinghouse for Federal Scientific and Technical Information, Springfield, Virginia 22151.

Blood Pressure Reprogramming Adapter Assists Signal Recording



The blood pressure signal contains two components that are mixed together in telemetry applications, a dc pressure signal and an ac (36 cps) Korotkoff sounds signal. Most tape recorders are incapable of recording the composite signal on the same channel because of their frequency response limitations.

A blood pressure reprogramming adapter has been designed to separate the two signals so that the Korotkoff sounds are recorded on one channel as received while the dc pressure signal is converted to FM and recorded on a second channel. This circuitry has the advantage over other conversion devices such

as rc multivibrators, square loop transformer oscillators, and voltage controlled oscillators, in its inherent linearity and low power drain.

Basically, the circuit consists of a differential dc amplifier that varies the output of a constant current generator that in turn varies the frequency of a unijunction transistor oscillator. Output of the oscillator is fed to a bistable flip-flop that produces a symmetrical output. The first five transistors form a high gain dc amplifier with Q₁ acting as a constant current source. Transistors Q₂ and Q_{2A} form a matched pair of NPN silicon planar transistors while Q₃ and

(continued overleaf)

Q_{3A} form a matched pair of PNP planar transistors and these are so connected that they provide high current gain and low temperature drift. Capacitors C₁ and C₂ across R₁ and R₂ limit the ac gain at 36 cps to approximately 1.6, which provides adequate signal while preventing interference to the oscillator. Transistor Q₄ and capacitor C₃ remove the Korotkoff sounds from the pressure ramp and apply them to output 1. Transistor Q_{3A} forms the second stage of the dc amplifier with Q₅ acting as its current source. Current in Q_{3A} is set by adjusting R₃ with the input shorted. The repetition rate of Q₆ is directly proportional to the current in Q_{3A} which, once set, is controlled by the differential voltage at its bases, originally determined by the input voltage. Output from Q₆ is in the form of sharp pulses which the tape recorder is unable to handle; consequently, the pulses are used to trigger the bistable flip-flop. Output of the bistable is a symmetrical square wave whose frequency is one half the unijunction oscillator frequency. Resistors R₄, R₅, R₆, and R₇ attenuate this

signal and provide the correct bias for compatibility with the tape recorder response.

Notes:

1. This circuitry draws only 2 ma from the -10v supply and 1 ma from the +10v supply and is absolutely linear from 10 cps to 100 cps.
2. Inquiries concerning this invention may be directed to:

Technology Utilization Officer
Manned Spacecraft Center
Houston, Texas 77058
Reference: B67-10475

Patent status:

This invention is owned by NASA, and a patent application has been filed. Royalty-free, nonexclusive licenses for its commercial use will be granted by NASA. Inquiries concerning license rights should be made to NASA, Code GP, Washington, D.C. 20546.

Source: Howard A. Vick
(MSC-265)